

# Gate Assignment 3

Rongala Arun Siddardha - AI20BTECH11019

Download latex-tikz codes from

[https://github.com/ArunSiddardha/EE3900/blob/main/GATE\\_ASSIGNMENT\\_3/main.tex](https://github.com/ArunSiddardha/EE3900/blob/main/GATE_ASSIGNMENT_3/main.tex)

## 1 PROBLEM(GATE EC 2004 Q.36)

A system is described by the following differential equation

$$\frac{d^2y(t)}{dt^2} + 3\frac{dy(t)}{dt} + 2y(t) = x(t) \quad (1.0.1)$$

is initially at rest. For the input  $x(t) = 2u(t)$  the output is given by

- 1)  $(1 - 2e^{-t} + e^{-2t})u(t)$
- 2)  $(1 + 2e^{-t} - e^{-2t})u(t)$
- 3)  $(0.5 + e^{-t} + 1.5e^{-2t})u(t)$
- 4)  $(0.5 + 2e^{-t} + 2e^{-2t})u(t)$

## 2 SOLUTION

**Lemma 2.1** (Table of Laplace Transforms).

Time Function $f(t) = \mathcal{L}^{-1}\{F(s)\}$	Laplace transform of $f(t)$ $F(s) = \mathcal{L}\{f(t)\}$
$u(t)$	$\frac{1}{s}, s > 0$
$g'(t)$	$sG(s) - g(0)$
$g''(t)$	$s^2G(s) - sg(0) - g'(0)$
$e^{-at}u(t)$	$\frac{1}{s+a}, s+a > 0$

**Lemma 2.2.** Linearity of Laplace Transform

$$\mathcal{L}\{af(t) + bg(t)\} = a\mathcal{L}\{f(t)\} + b\mathcal{L}\{g(t)\} \quad (2.0.1)$$

From Lemma-2.1 Laplace transform of  $x(t) = 2u(t)$  is given by

$$X(s) = \frac{2}{s} \quad (2.0.2)$$

Since initially it is at rest. Laplace Transform of (1.0.1) gives

$$s^2Y(s) + 3sY(s) + 2Y(s) = X(s) \quad (2.0.3)$$

$$Y(s) = \frac{2}{s(s^2 + 3s + 2)} \quad (2.0.4)$$

$$= \frac{1}{s+2} + \frac{1}{s} + \frac{-2}{s+1} \quad (2.0.5)$$

$$(2.0.6)$$

From Lemma-2.1. Inverse Laplace transform of  $Y(s)$  is given by

$$y(t) = -2e^{-t}u(t) + e^{-2t}u(t) + 1u(t) \quad (2.0.7)$$

$$= (-2e^{-t} + e^{-2t} + 1)u(t) \quad (2.0.8)$$

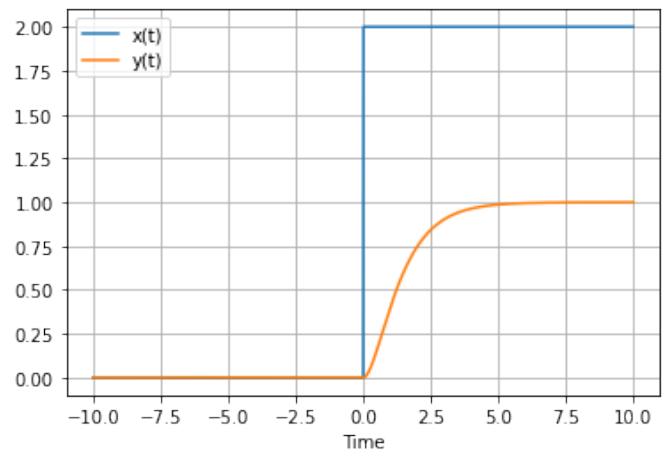


Fig. 4: Plot of input and output responses

∴ The required **option is A.**

Building RLC circuit that satisfies (1.0.1).


Assume ,

$$\frac{R}{L} = 3 \quad (2.0.9)$$

$$LC = \frac{1}{2} \quad (2.0.10)$$

$$\text{Input : } x(t) \quad (2.0.11)$$
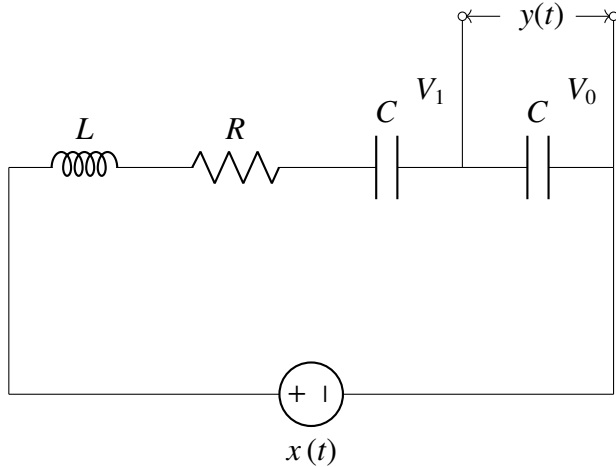
$$\text{Output : } y(t) = V_1 - V_0 \quad (2.0.12)$$



Using the KVL law

$$x(t) - V_L(t) - V_R(t) - V_C(t) - V_C(t) = 0 \quad (2.0.13)$$

And,

$$y(t) - V_C(t) = 0 \quad (2.0.14)$$

Because of the linearity, KVL equation in the s-domain produces

$$X(s) - V_L(s) - V_R(s) - V_C(s) - V_C(s) = 0 \quad (2.0.15)$$

And,

$$Y(s) = V_C(s) \quad (2.0.16)$$

Converting the  $i - v$  relationships of resistors, capacitors, inductors to the s-domain (laplace domain) using the integration and derivative properties.

$$\text{Resistor : } V_R(t) = Ri_R(t) \rightarrow V_R(s) = Ri_R(s) \quad (2.0.17)$$

$$\begin{aligned} \text{Capacitor : } V_C(t) &= \int_0^t i_C(\tau) d\tau \rightarrow \\ V_C(s) &= \frac{1}{sC} I_C(s) + \frac{V_C(0)}{s} \end{aligned} \quad (2.0.18)$$

$$\text{Inductor : } V_L(t) = L \frac{di_L}{dt} \rightarrow$$

$$V_L(s) = sLI_L(s) - Li_L(0) \quad (2.0.19)$$

$\therefore$  The series is a series circuit current passing through all the devices is same.

And taking the into the condition that initial state is 0 for the system. And then substituting (2.0.17), (2.0.18), (2.0.19) in (2.0.15)

$$X(s) - sLI(s) - RI(s) - \frac{1}{sC}I(s) - \frac{1}{sC}I(s) = 0 \quad (2.0.20)$$

$$\frac{X(s)}{sL + R + \frac{2}{sC}} = I(s) \quad (2.0.21)$$

similarly,

$$Y(s) = \frac{1}{sC} I(s) \quad (2.0.22)$$

Using (2.0.21), (2.0.22), (2.0.9), (2.0.10) we get,

$$Y(s) = \frac{1}{(s^2 + 3s + 2)} X(s) \quad (2.0.23)$$

which is same as (2.0.3)

Taking the inverse laplace transform we get (1.0.1).

**Verifying our solution using ngspice plot:**

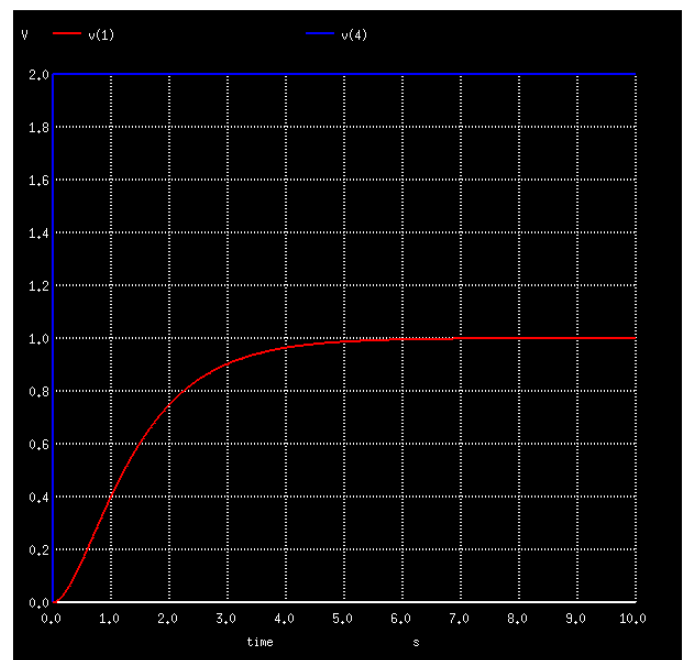


Fig. 4: Plot obtained using ngspice input:blue and output:red

Combining our theoretical plot and ngspice plot  
:

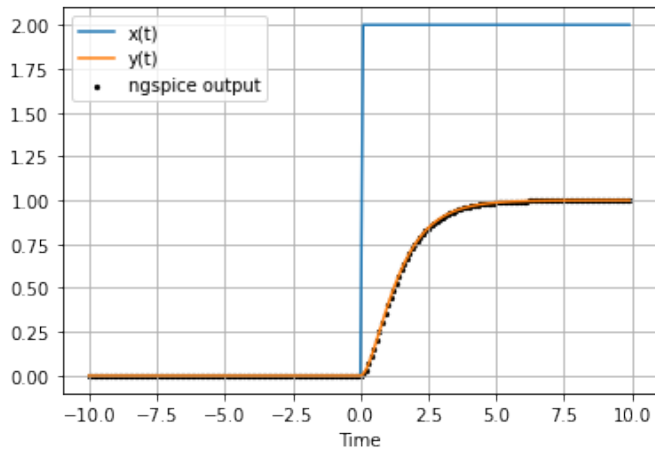


Fig. 4: Plotting theoretical input/output and ngspice output in the same graph